
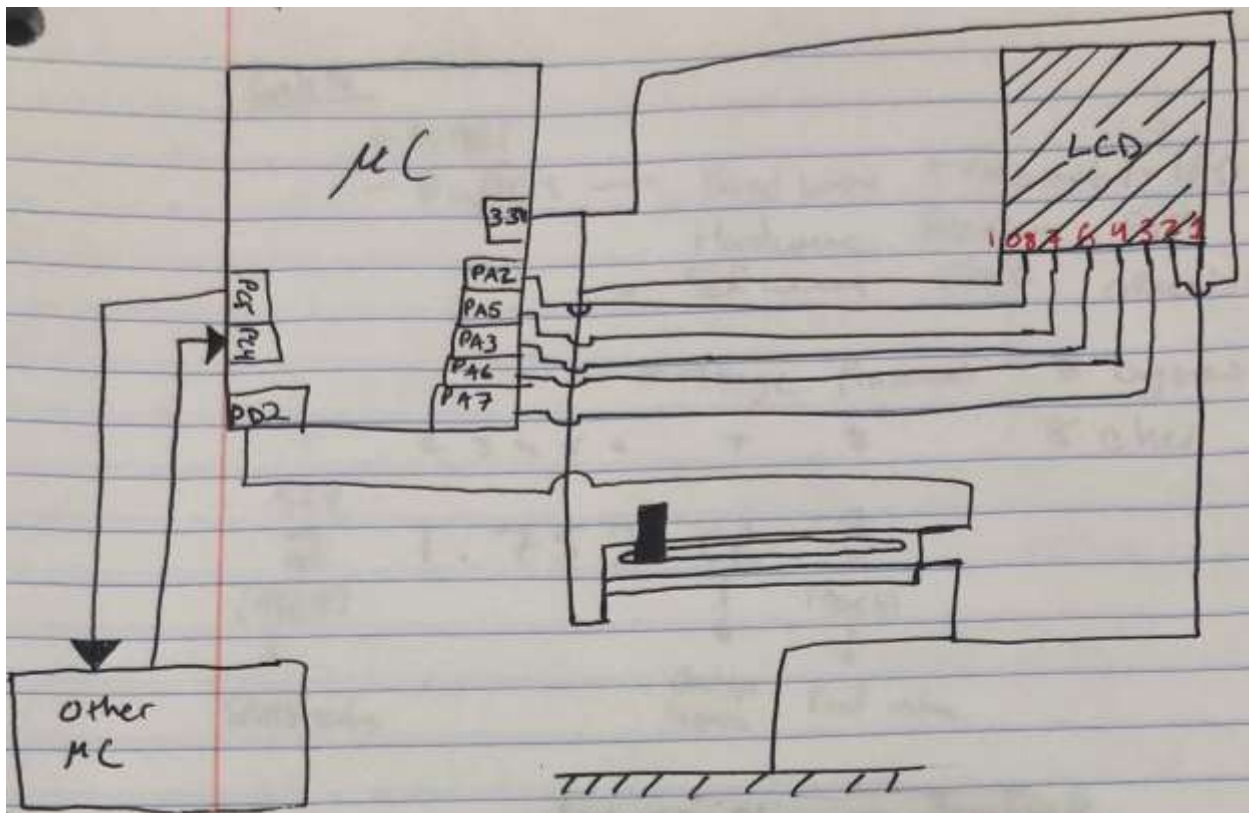


Lab 9 Deliverables


1. Circuit diagram

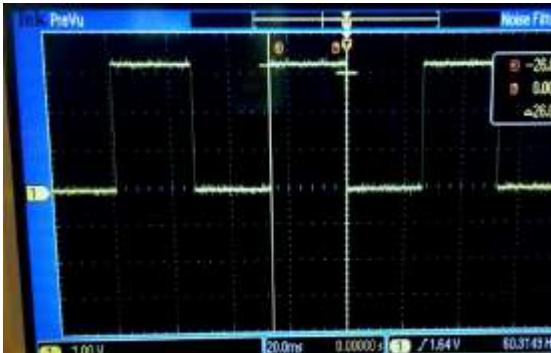

2. Scope Readings



SysTick Interrupt

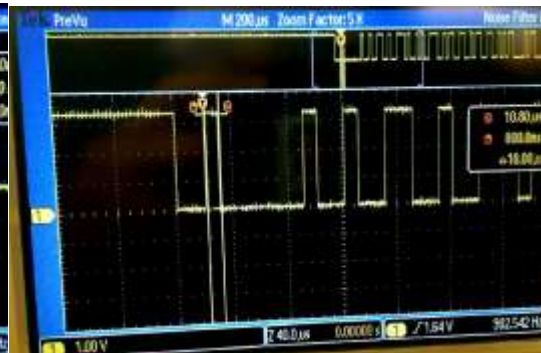

Serial Interrupt (UART)